

Physics 231

Lecture 3: Op Amps I

Eric Landahl

DePaul University Physics Department

April 28, 2025

Table of Contents

Thevenin Equivalent Circuits

- Analysis

- The Voltage Divider Source

- The Loading Problem

The Op Amp

- Basic Properties


- Follower/Buffer

- Comparator

- Amplifier (non-inverting)


Thevenin Equivalent Circuits: Analysis

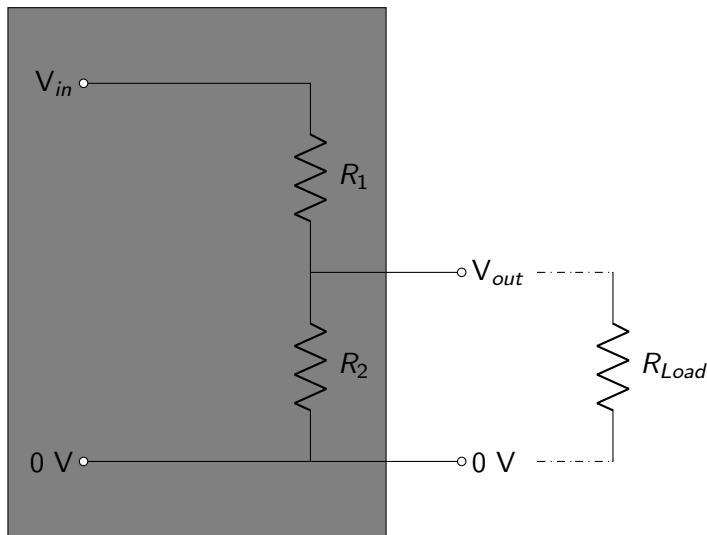Replace the entire source with a "black box" with an equivalent voltage and an equivalent resistance in series.



Thevenin Equivalent Circuits: Analysis

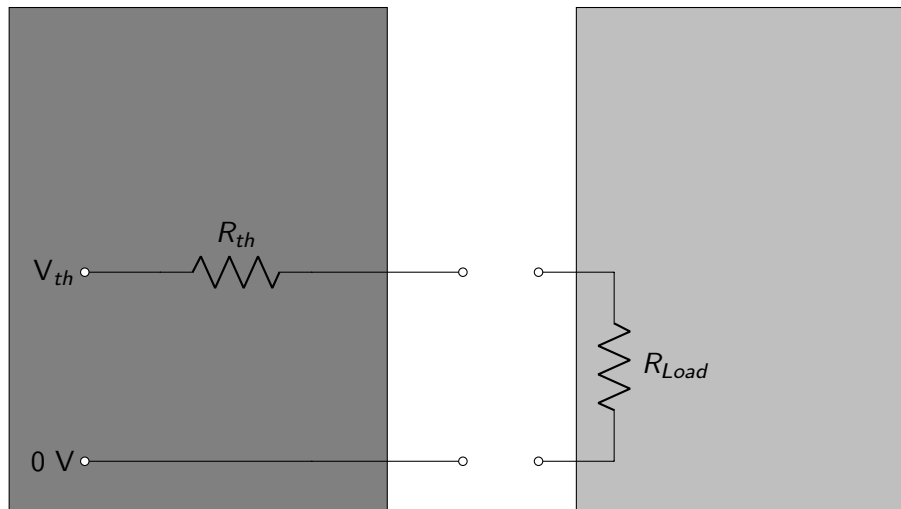
The “Thevenin Equivalent” Circuit is defined to be the one where the output voltage $V_{out} = \frac{V_{th}}{2}$ when connected to a load $R_{Load} = R_{th}$. Every power supply has a V_{th} and R_{th} .



Thevenin Equivalent Circuits: Analysis


Step 1: Determine the voltage across the outputs without the load attached (as an open circuit). This open circuit voltage is V_{th} .

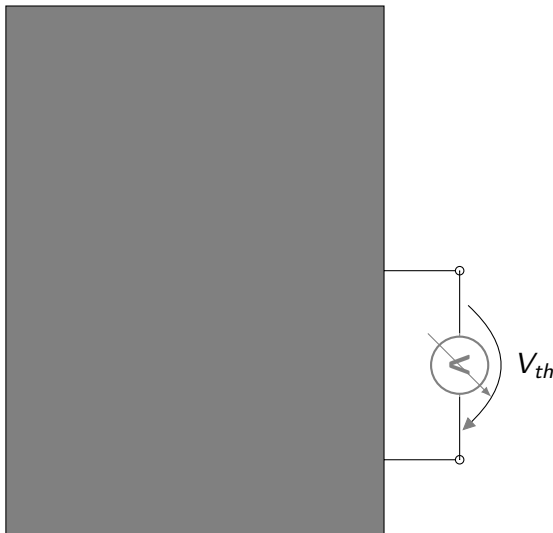Remember, the voltmeter draws no current.



Thevenin Equivalent Circuits: Analysis

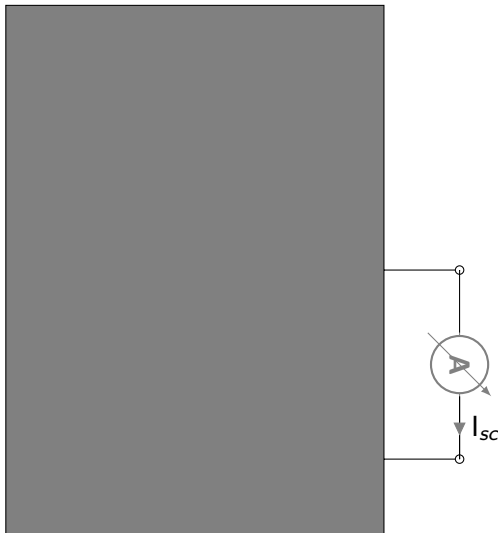
Step 2: Determine the current through the outputs when they are shorted. This short circuit current is I_{sc} . Remember, the ammeter has zero resistance and is a short.



Thevenin Equivalent Circuits: Analysis

Step 3. Calculate the equivalent (or source, or Thevenin) resistance by dividing the open-circuit voltage by the short-circuit current.

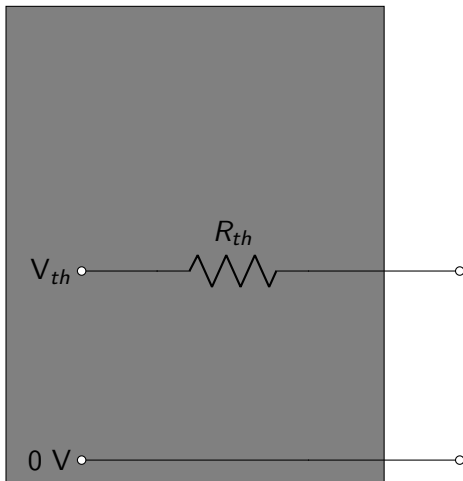
$$R_{th} = \frac{V_{th}}{I_{sc}} \quad (1)$$



Thevenin Equivalent Circuits: Analysis

Step 4. The output voltage V_{out} can now be determined for any load resistance R_{Load} by using the voltage divider equation.
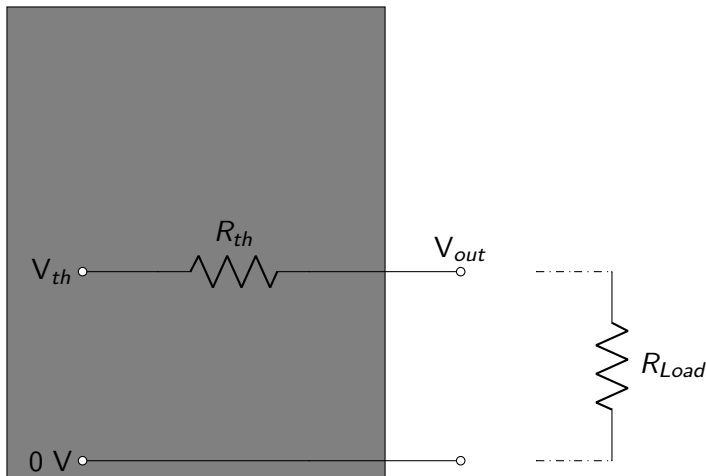
$$V_{out} = \left(\frac{R_{Load}}{R_{Load} + R_{th}} \right) V_{th} \quad (2)$$



Thevenin Equivalent Circuits: Analysis

Special cases of load resistance:

$$V_{out} = \left(\frac{R_{Load}}{R_{Load} + R_{th}} \right) V_{th} \quad (3)$$


1. If $R_{Load} = \infty$ (no load), the circuit is open and $V_{out} = V_{th}$
2. If $R_{Load} = 0$, the circuit is shorted and $V_{out} = 0$
3. If $R_{Load} = R_{th}$ then $V_{out} = \frac{V_{th}}{2}$
4. If $R_{Load} \gg R_{th}$ then $V_{out} = V_{th}$, or a “good load”
5. If $R_{Load} \approx R_{th}$ then $V_{out} < V_{th}$, or a “poor load”

Always check your answer by Property 3:

Loading with the source resistance halves the output voltage.

Thevenin Equivalent Circuits: The Voltage Divider Source

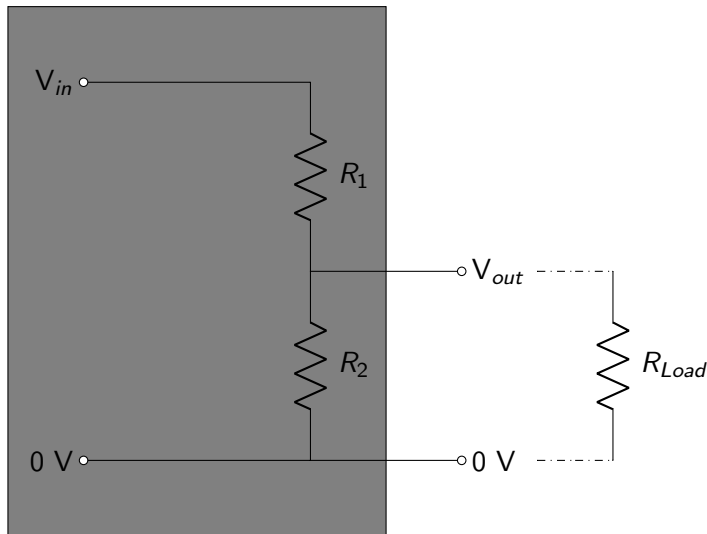
$$\frac{1}{R_{th}} = \frac{1}{R_1} + \frac{1}{R_2} \quad \text{or} \quad R_{th} = \frac{R_1 R_2}{R_1 + R_2} \quad (4)$$



Thevenin Equivalent Circuits: The Voltage Divider Source


Check by first inserting the calculated R_{Load}

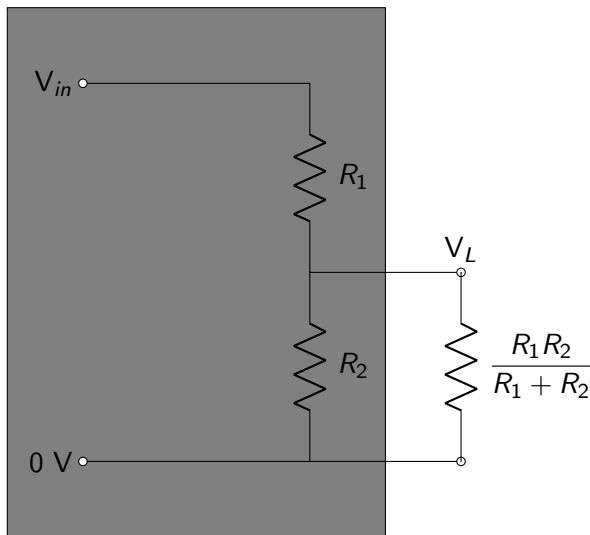Then V_{out} drops to the “Loaded” value V_L :




Thevenin Equivalent Circuits: The Voltage Divider Source

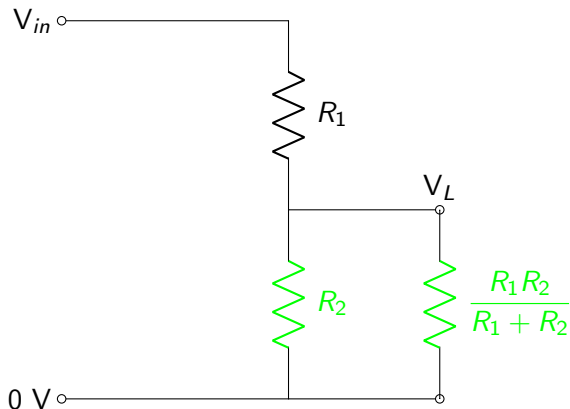Next, turning R_{Load} and R_2 into an equivalent resistor



Thevenin Equivalent Circuits: The Voltage Divider Source

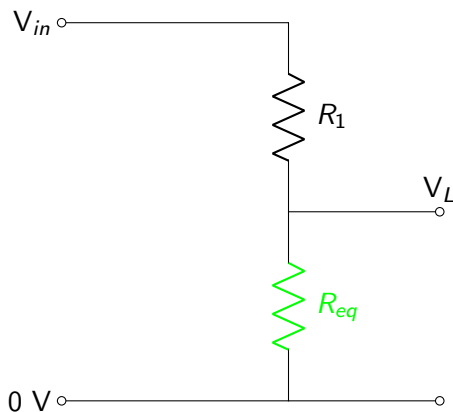
$$\frac{1}{R_{eq}} = \frac{1}{R_2} + \frac{1}{R_{th}} = \frac{1}{R_2} + \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{2}{R_2} + \frac{1}{R_1} \quad (5)$$



Thevenin Equivalent Circuits: The Voltage Divider Source

Then applying the voltage divider equation
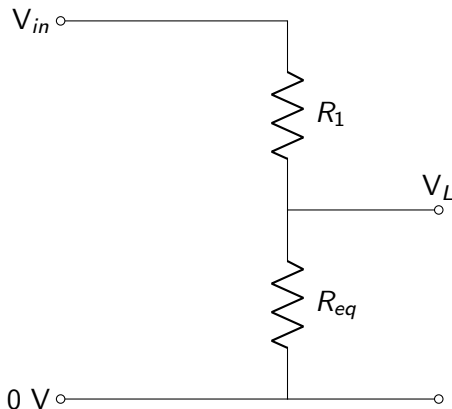
$$V_L = \left(\frac{R_{eq}}{R_{eq} + R_1} \right) V_{in} \quad (6)$$



Thevenin Equivalent Circuits: The Voltage Divider Source

Simplifying using algebra:

$$V_L = \left(\frac{R_{eq}}{R_{eq} + R_1} \right) V_{in} \quad (7)$$

$$= \left(\frac{R_{eq} R_1}{R_{eq} + R_1} \right) \frac{V_{in}}{R_1} \quad (8)$$

$$= \left(\frac{1}{R_1} + \frac{1}{R_{eq}} \right)^{-1} \frac{V_{in}}{R_1} \quad (9)$$

$$= \left(\frac{1}{R_1} + \frac{2}{R_2} + \frac{1}{R_1} \right)^{-1} \frac{V_{in}}{R_1} \quad (10)$$


$$= \left(\frac{2}{R_1} + \frac{2}{R_2} \right)^{-1} \frac{V_{in}}{R_1} \quad (11)$$

$$= \left(\frac{R_1 R_2}{R_1 + R_2} \right) \frac{V_{in}}{2 R_1} \quad (12)$$

$$V_L = \left(\frac{R_2}{R_1 + R_2} \right) \frac{V_{in}}{2} = \frac{V_{out}}{2} \quad (13)$$


Thevenin Equivalent Circuits: The Loading Problem

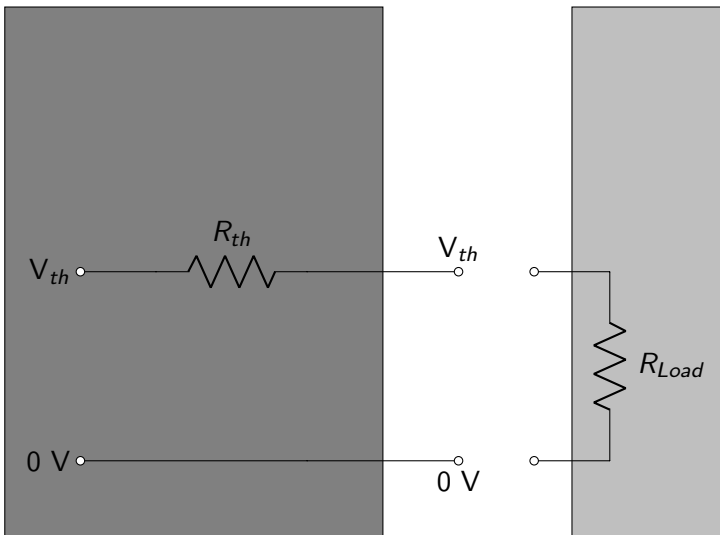Any circuit can be split into a Source and a Load.




Thevenin Equivalent Circuits: The Loading Problem

But connecting them changes the voltage.

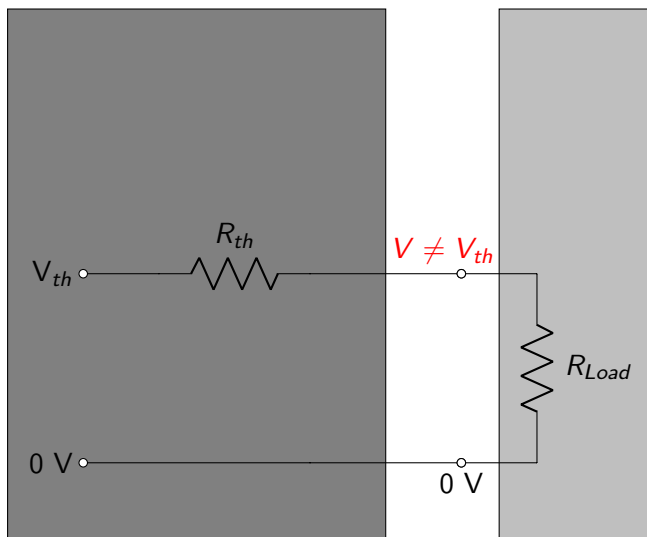

Thevenin Equivalent Circuits: The Loading Problem

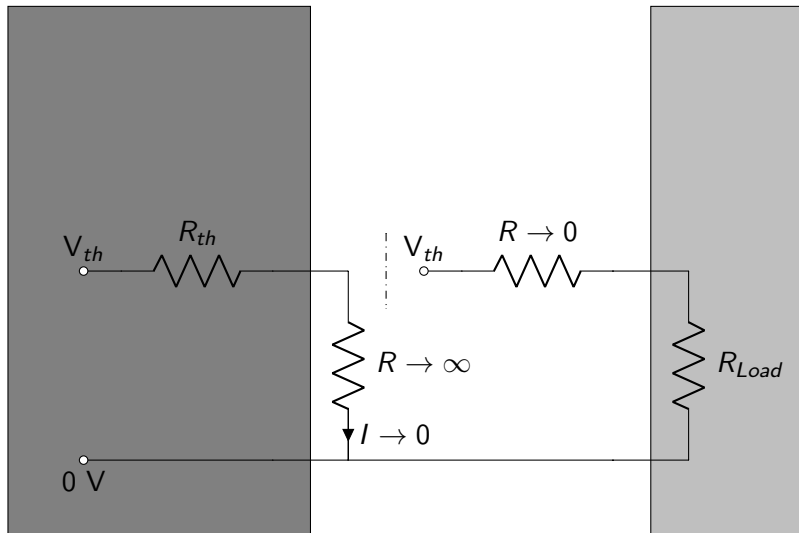We need a “matchmaker”: a component that looks like a high resistance when viewed from the Source, but looks like a low resistance when viewed from the Load.




The Op Amp: Basic Properties

The input leads draw no current


The output has zero source resistance

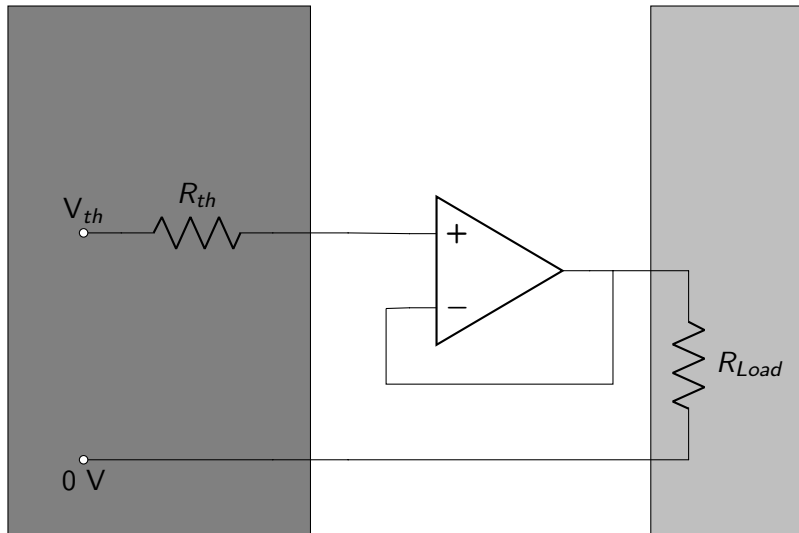The output attempts to make the input voltages the same




The Op Amp: Follower/Buffer

$$V_{out} = V_{in}$$

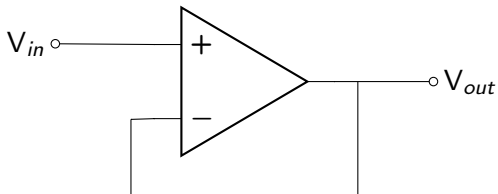

The Op Amp: Comparator
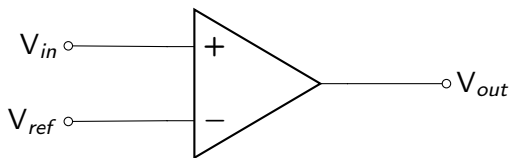
$$V_{out} \rightarrow \begin{cases} HIGH, & \text{if } V_{in} > V_{ref}. \\ LOW, & \text{if } V_{in} < V_{ref}. \end{cases}$$



The Op Amp: Amplifier (non-inverting)

$$V_{out} = \left(1 + \frac{R_1}{R_2}\right) V_{in}$$

