

Physics 231

Lecture 4: Op Amps II

Eric Landahl

DePaul University Physics Department

May 5, 2025

Table of Contents

The Op-Amp Golden Rules

Basic Op-Amp Circuits

- Follower/Buffer

- Comparator

- Amplifier (non-inverting)

- Amplifier (inverting)

- Differential Amplifier

2 bit Analog-to-Digital Converter (ADC)

The Op-Amp Golden Rules:

The input leads draw no current

High input resistance

The output can produce enough current to drive any load


Low output resistance

The output tries to make the input voltages the same

Operational amplifiers are usually used with feedback

Basic Op-Amp Circuits: Follower/Buffer


$$V_{out} = V_{in}$$

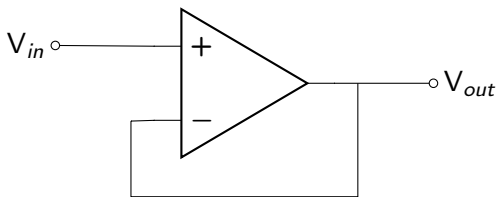

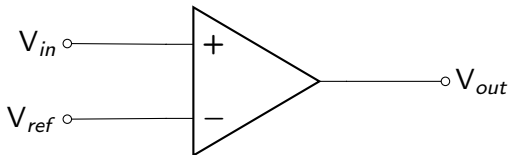Task: Make a follower that buffers negative voltages as well using an LM 741 op-amp.

Basic Op-Amp Circuits: Comparator


$$V_{out} \rightarrow \begin{cases} \text{HIGH}, & \text{if } V_{in} > V_{ref}. \\ \text{LOW}, & \text{if } V_{in} < V_{ref}. \end{cases}$$



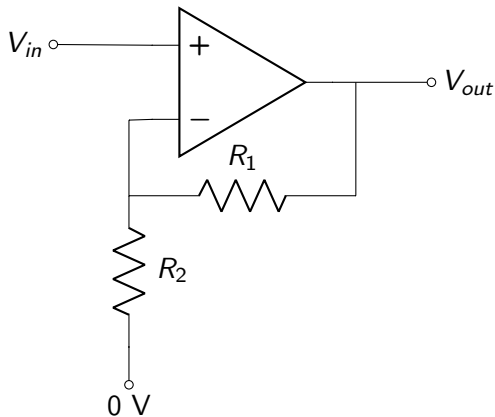Task: Make an comparator that outputs HIGH when $V_{in} > V_{ref}$.
Set V_{in} using a potentiometer.

Basic Op-Amp Circuits: Amplifier (non-inverting)


$$V_{out} = \left(1 + \frac{R_1}{R_2}\right) V_{in}$$



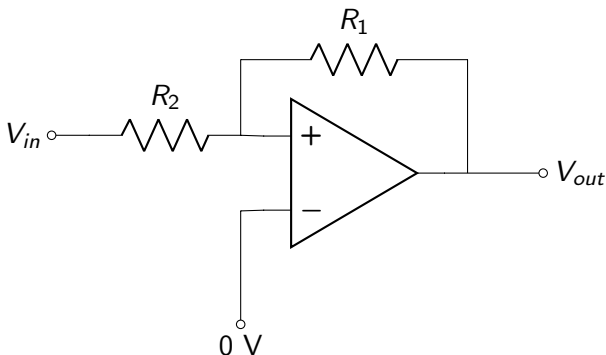Task: Derive the gain equation for this amplifier.

Hint: Adapt the voltage divider equation.


Basic Op-Amp Circuits: Amplifier (inverting)



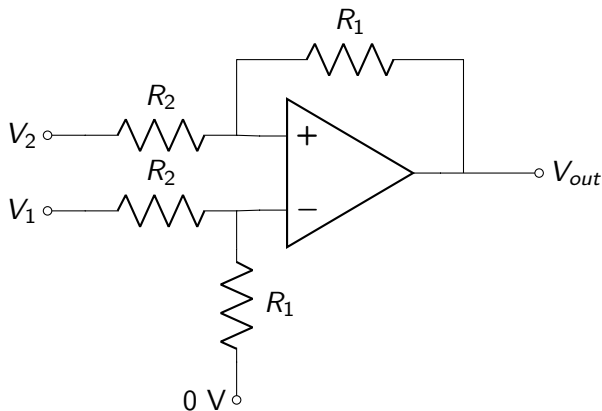Task: Derive the gain equation for this amplifier. Build and test it.
What might this be used for? What is a disadvantage?

Basic Op-Amp Circuits: Differential Amplifier


$$V_{out} = \frac{R_1}{R_2} (V_2 - V_1)$$



Task: Build and test.

Adapt to amplify small changes around a reference of 2.5 V.

2 bit Analog-to-Digital Converter (ADC):

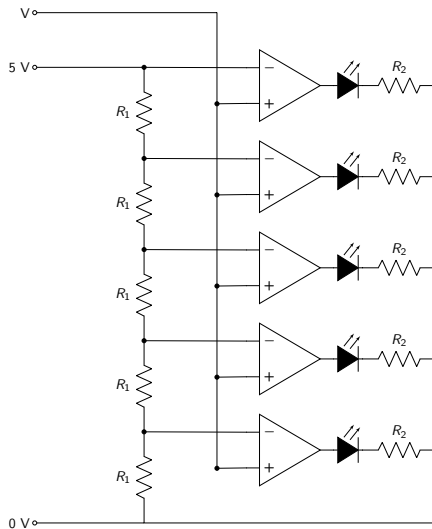

How would you choose appropriate R_1 and R_2 ?